

# Modelling and control summaries




by Anthony Rossiter

## Modelling principles and analogies 1:
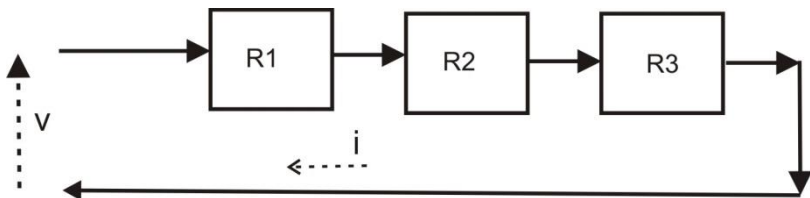
### Modelling resistors in series

Consider an electrical circuit with supplied voltage  $v(t)$ , a set of resistors arranged in series (such as in figure here) and a current flow  $i(t)$ .

What is the relationship between the current, the voltage and the resistances?




These notes will give a brief overview of the foundational assumptions required to answer this question.

#### Model for a single resistor


The current flow is proportional to the voltage. Specifically, the dependence can be expressed as:

$$v = iR_1$$

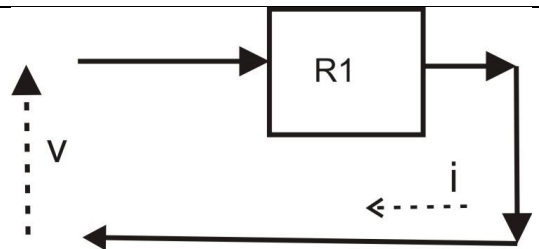
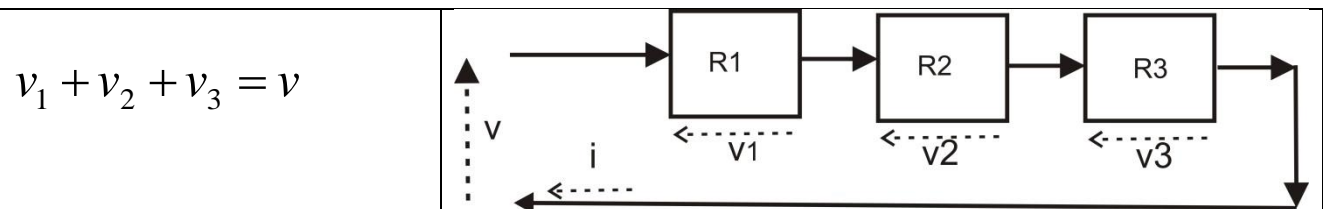
#### Kirchhoff's Voltage Law

All the voltages acting round a loop of a circuit must sum algebraically to zero. *Algebraically* means attributing opposite signs to voltages acting in opposite directions, say, clockwise and counter clockwise respectively. Hence, for the general loop illustrated below:




**Assumption:** Electrical components in series share the same current.

Combining the rule for a single resistor with Kirchhoff's voltage law and the assumption, one can now derive a model for many resistors in series.


**Model for a two resistors in series**

Modelling simply requires a statement of each observation above and then a simplification of the resulting equations.
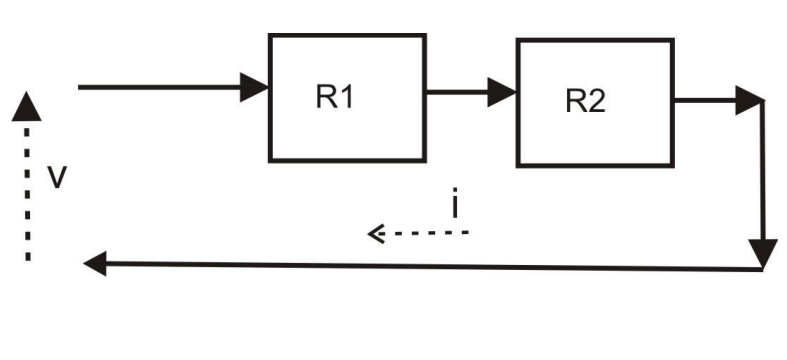
<p>1. The voltage across resistor R1</p> $v_1 = iR_1$ <p>2. The voltage across resistor R2</p> $v_2 = iR_2$ <p>3. Kirchhoff's voltage law:</p> $v_1 + v_2 = v$	
<p>Combining these three equations gives:</p> $iR_1 + iR_2 = v \Rightarrow v = i(R_1 + R_2)$	

**Model for a three resistors in series**

Modelling requires a statement of each observation above and then a simplification of the resulting equations.

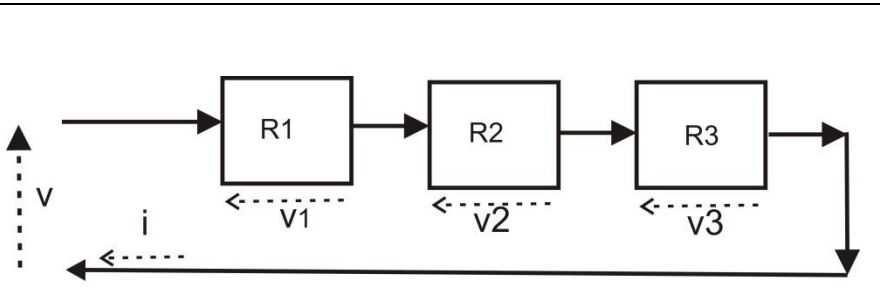
<p>1. The voltage across resistor R1</p> $v_1 = iR_1$ <p>2. The voltage across resistor R2</p> $v_2 = iR_2$ <p>3. The voltage across resistor R3:</p> $v_3 = iR_3$ <p>3. Kirchhoff's voltage law:</p> $v_1 + v_2 + v_3 = v$	 <p style="color: red; font-weight: bold;">Combining these four equations gives:</p> $iR_1 + iR_2 + iR_3 = v \Rightarrow v = i(\underbrace{R_1 + R_2 + R_3}_{R_t})$
---	---

**Remark:** It is clear that for n resistors in series, the corresponding model will be:

$$iR_1 + iR_2 + \dots + iR_n = v \Rightarrow v = i(\underbrace{R_1 + R_2 + \dots + R_n}_{R_t})$$
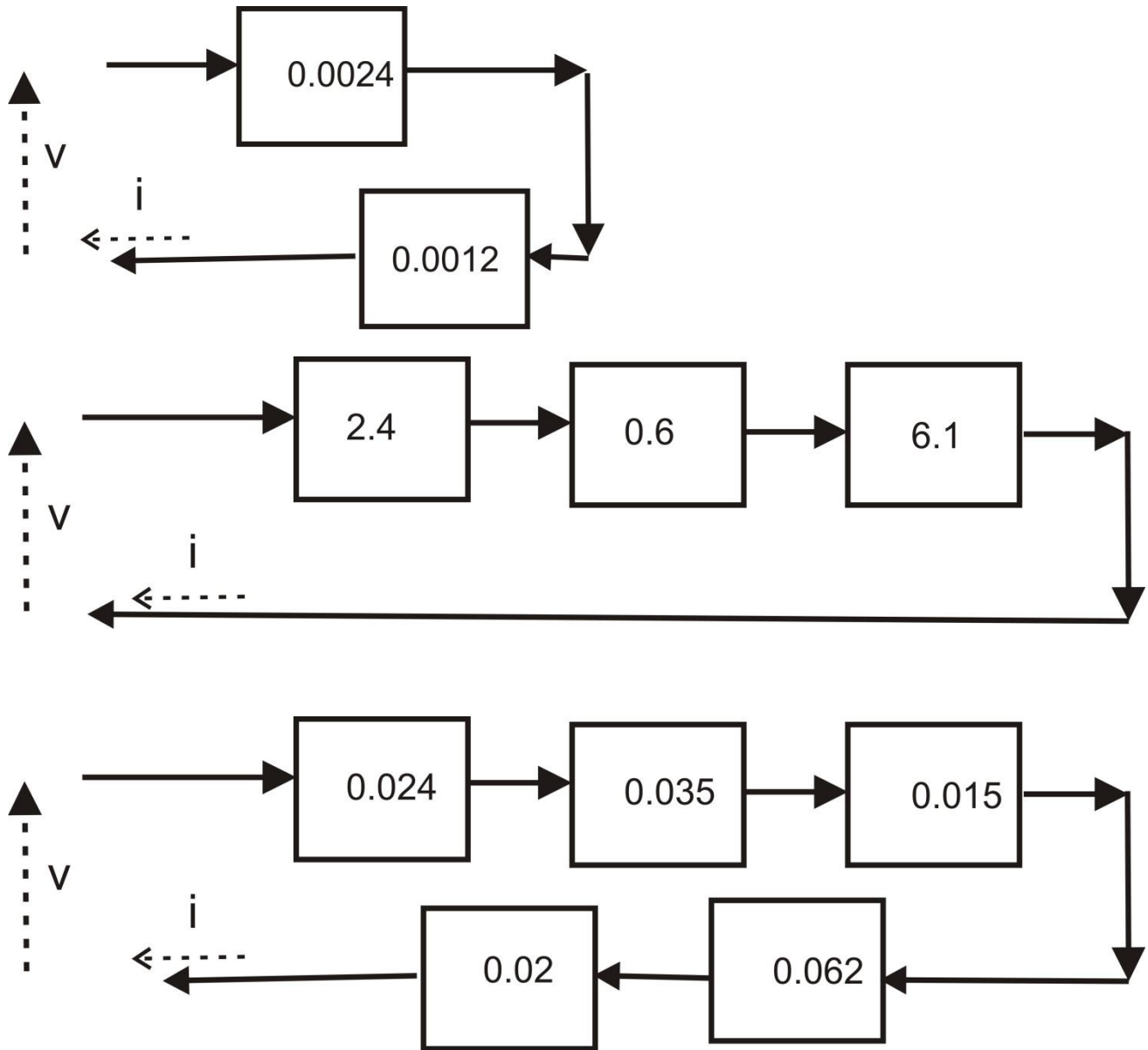
## Tutorial questions

Find the overall circuit resistance for the following circuits. (Any numbers given represent the resistance in ohms).



ANSWERS: (i)  $0.0036$ ohms (ii)  $9.1$ ohms; (iii)  $0.156$ ohms