

# Modelling and control summaries




by Anthony Rossiter

## Modelling principles and analogies 4:
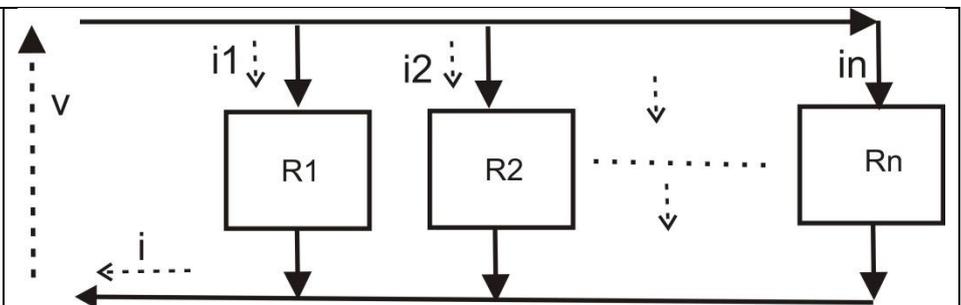
### Modelling resistors in parallel

Consider an electrical circuit with supplied voltage  $v(t)$ , a set of resistors arranged in parallel (such as in figure here) and an overall current flow  $i(t)$ .

What are the relationships between the currents, the applied voltage and the resistances?




These notes will give a brief overview of the foundational assumptions required to answer this question.

#### Model for a single resistor

The current flow is proportional to the voltage. Specifically, the dependence can be expressed as:


$$v = iR_1$$

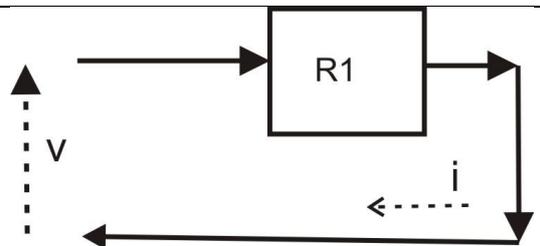

#### Kirchhoff's Current Law

All the currents acting at a single point must add to zero.

$$i_1 + i_2 + \dots + i_n = 0$$

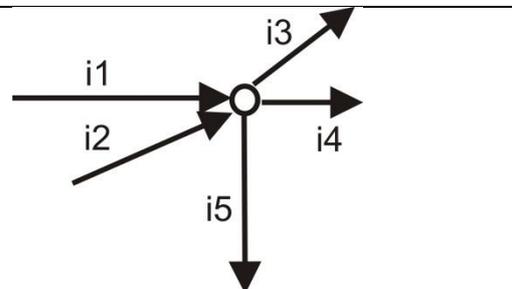

**Assumption:** Electrical components in parallel share the same voltage.

Combining the rule for a single resistor with Kirchhoff's current law and the assumption, one can now derive a model for many resistors in parallel.

**Model for a two resistors in parallel**

Modelling requires a statement of each observation above and a simplification of the resulting equations.

<p>1. The current across resistor R1  <math>v = i_1 R_1</math></p> <p>2. The current across resistor R2  <math>v = i_2 R_2</math></p> <p>3. Kirchhoff's current law:  <math>i_1 + i_2 = i</math></p>	
<p>Combining these three equations gives:</p> $\frac{v}{R_1} + \frac{v}{R_2} = i_1 + i_2 = i \Rightarrow v = i \left( \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \right); R_T = \left( \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \right)$	



**Model for a many resistors in parallel**

Modelling requires a statement of each observation above and a simplification of the resulting equations.

<p>1. The current across resistor R1  <math>v = i_1 R_1</math></p> <p>2. The current across resistor Rj  <math>v = i_j R_j</math></p> <p>3. Kirchhoff's current law:  <math>i_1 + \dots + i_n = i</math></p>	
<p style="color: red;">Combining these equations gives:</p> $\frac{v}{R_1} + \frac{v}{R_2} + \dots + \frac{v}{R_n} = i_1 + i_2 + \dots + i_n = i \Rightarrow v = i \left( \frac{1}{\underbrace{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}_{R_T}} \right)$	
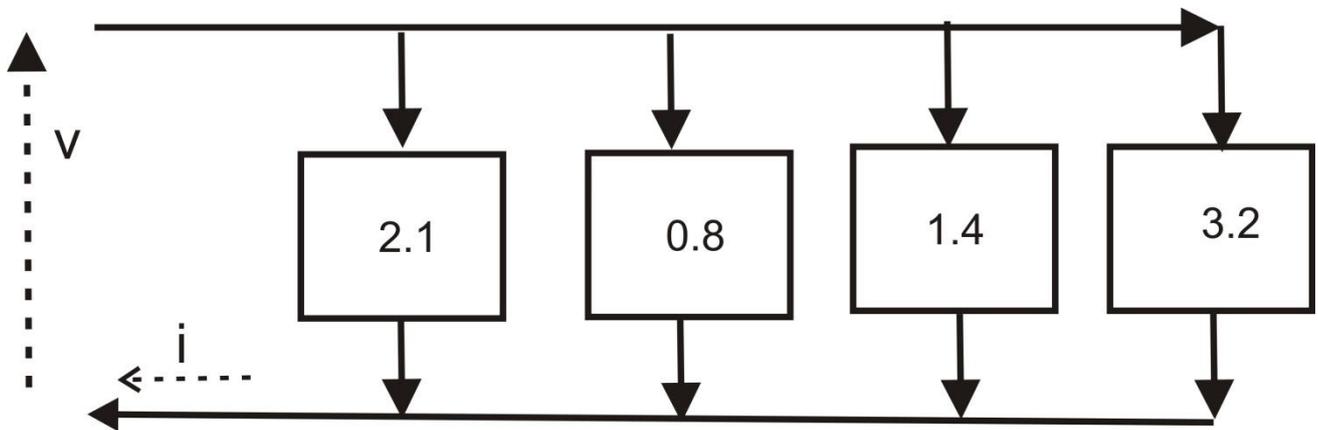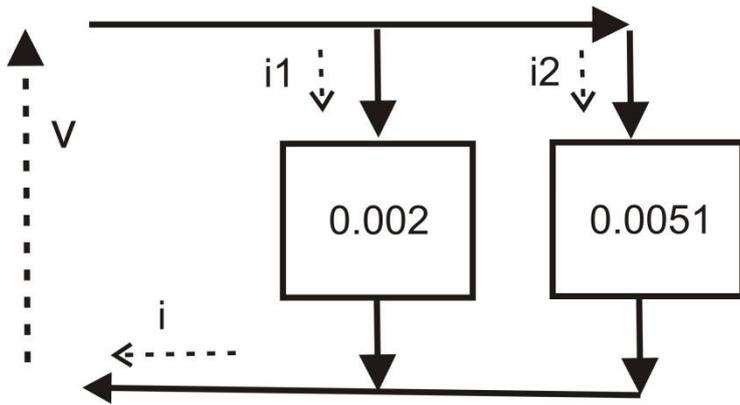
## Tutorial questions

Find the overall circuit resistance for the following circuits. (Any numbers given represent the resistance in ohms).



Which has greatest resistance from: (i) a circuit with two equal resistors in series and (ii) a circuit with 5 equal resistors in parallel?

- In general, does adding a resistor in parallel reduce or increase overall resistance?
- In general, does adding a resistor in series reduce or increase overall resistance?

ANSWERS: (i) 0.0014ohms (ii) 0.3632ohms;